

ECE 209: *Circuits and Electronics Laboratory*

Lab 3: Operational Amplifiers and First-Order Circuits Quiz (100 points)

Description. This quiz tests your comprehension of the introductory material on operational amplifier circuits and first-order LTI systems. This quiz is **closed book** and **closed notes**.

Problem Q3-1: Operational Amplifier Circuit (20 points)

The circuit in Figure Q3-1.1 uses an *ideal* operational amplifier in a common configuration.

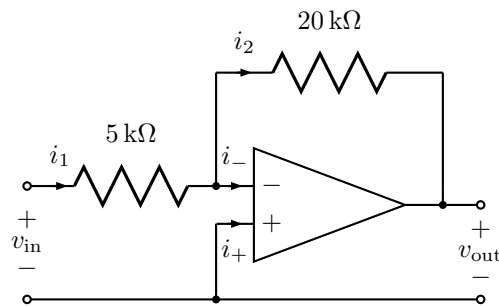


Figure Q3-1.1: Operational amplifier circuit.

The circuit produces an output v_{out} that is an amplified version of the input v_{in} . That is,

$$v_{\text{out}} = G \times v_{\text{in}}.$$

1. What is the gain G of the circuit in Figure Q3-1.1? Make sure you specify the **sign** of the gain. (20 points)

SOLUTION

An operational amplifier is a special kind of differential amplifier, and so its output

$$v_{\text{out}} = A \times (v_+ - v_-).$$

That is, $(v_+ - v_-) = v_{\text{out}}/A$. However, because it is an *ideal operational* amplifier, the gain A is assumed to be practically infinite, and so if we also assume that v_{out} is finite, then $v_+ - v_- \approx 0$ V. Further, because $v_+ = 0$ V, then

$$v_- \approx v_+ = 0 \text{ V}.$$

Therefore,

$$i_1 \approx \frac{v_{\text{in}}}{5 \text{ k}\Omega}.$$

For an *ideal operational* amplifier, the current $i_- \approx 0$ A, and so $i_2 \approx i_1 \approx v_{\text{in}}/(5 \text{ k}\Omega)$, and

$$\begin{aligned} v_{\text{out}} &= v_- - i_2 \times 20 \text{ k}\Omega \\ &\approx -i_1 \times 20 \text{ k}\Omega \\ &\approx -\frac{20 \text{ k}\Omega}{5 \text{ k}\Omega} v_{\text{in}} \\ &= -4 \times v_{\text{in}}. \end{aligned}$$

So gain $G = -4$. The circuit in Figure Q3-1.1 is a **inverting amplifier** with a gain of magnitude 4.

Problem Q3-2: Step Response (20 points)

At time $t = 0$, a unit step is placed onto the input of a first-order linear-time-invariant (LTI) system with zero initial conditions, and the output of the system follows the trajectory shown in Figure Q3-2.1.

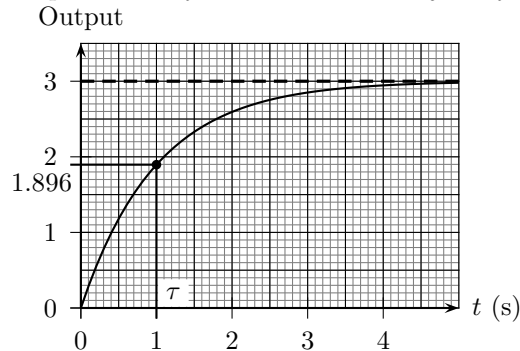


Figure Q3-2.1: Unit step response from first-order LTI system.

To answer the following questions, it may be helpful to know that

$$e^{-1} \approx 0.368 \quad \text{and} \quad 3e^{-1} \approx 1.104 \quad \text{and} \quad 1 - e^{-1} \approx 0.632 \quad \text{and} \quad 3 - 3e^{-1} \approx \boxed{1.896}$$

2. Estimate the time constant τ of the first-order LTI system. (10 points)

SOLUTION

The time constant is the time needed for the circuit to settle *within* e^{-1} (i.e., 37%) of its final value after a step input. The final value of this step response is 3, and so the time constant τ is the time when the output crosses $3 \times (1 - e^{-1})$ or 1.896. From the graph, that $\tau \approx 1$ s.

3. What kind of filter is this first-order LTI system? (10 points)

SOLUTION

The filter is unable to track the sharp edge of the input, but it tracks the slow constant trend of the input perfectly. Hence, it is a **low-pass filter**.

4. **BONUS:** If $H(s)$ is the transfer function of this LTI system, then what is $H(0)$? (5 points)

SOLUTION

The value of $H(s)$ when $s = 0$ is the DC gain of the filter. The DC component of the input is 1, and the DC component of the output is ~ 3 , and so the DC gain is 3. That is, $H(0) = 3$. Also note that by the **final value theorem** (FVT), $3 = \lim_{t \rightarrow \infty}$ “step response” $\stackrel{\text{FVT}}{=} \lim_{s \rightarrow 0} s(1/s)H(s) = H(0)$.

5. **BONUS:** What is the transfer function $H(s)$ of this LTI system? (10 points)

SOLUTION

Every first order low-pass filter takes the form

$$K_{\text{DC}} \frac{1}{1 + \tau s} = \frac{K_{\text{DC}}}{\tau} \frac{1}{s + \frac{1}{\tau}}, \quad \text{and so because } K_{\text{DC}} = 3 \text{ and } \tau = 1, \quad \boxed{H(s) = \frac{3}{s + 1}}$$

You get the same answer if you either:

- Take the Laplace transform of the step response and multiply by s . That is, $H(s) = s \times \mathcal{L}\{3(1 - e^{-t})\} = 3s(1/s - s/(s+1)) = 3s/(s(s+1)) = 3/(s+1)$.
- Take the Laplace transform of the impulse response, which is the derivative of the step response. That is, $H(s) = \mathcal{L}\{3e^{-t}\} = 3/(s+1)$.

Problem Q3-3: Filter Analysis (60 points)

A first-order passive LTI system implemented with a resistor with resistance R and a capacitor with capacitance C is shown in Figure Q3-3.1.

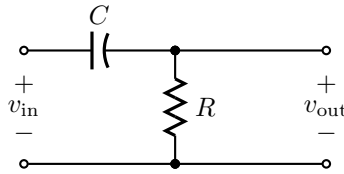


Figure Q3-3.1: First-order passive LTI system.

The following questions refer to the LTI system in Figure Q3-3.1.

6. What is the $V_{\text{out}}(s)/V_{\text{in}}(s)$ transfer function of this system? (20 points)

SOLUTION

Recall that the capacitor's transfer characteristic is $i_C(t) = Cv'_C(t)$ where $v'_C(t)$ is the time derivative of the capacitor voltage v_C and i_C is the capacitor current. So for any $v_C(t) \triangleq \sin(\omega t)$, $i_C(t) = \omega \cos(\omega t)$. Hence, when the frequency ω is fixed, $\max\{v_C\}/\max\{i_C\} = 1/\omega$; the capacitor acts like a resistor with resistance $1/\omega$, except that it stores energy rather than dissipating it. *Mathematically* speaking, impedance acts like frequency-dependent resistance.

So the impedance of a capacitor with capacitance C is $1/(sC)$, and the circuit is a voltage divider that divides the total impedance $R + 1/(sC)$ across the resistance R . The transfer function

$$H(s) \triangleq \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{RC}} = \frac{sRC}{sRC + 1}.$$

7. What kind of filter is this system? (20 points)

SOLUTION


Because $H(s)$ has a zero at $s = 0$ and a pole at $s = 1/(RC)$, then $H(0) = 0$ and $|H(j\omega)| \rightarrow 1$ as $\omega \rightarrow \infty$. So the circuit is a **high-pass filter**.

8. What is the time constant τ of this first-order LTI system? (20 points)

SOLUTION

The time constant of a first-order LTI system is the inverse of its single pole. So $\tau = RC$.

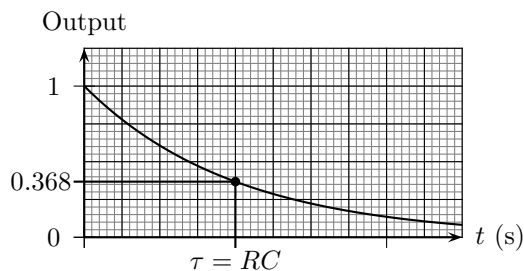9. **BONUS:** Sketch the zero-state unit step response of this first-order LTI system. Show the **time constant** τ on your sketch, and make sure the **gain** of the system is clear. (10 points)



SOLUTION

Because the capacitor is initially discharged, $v_{\text{out}}(0+) = v_{\text{in}}(0+) = 1$. As it charges, the output decays as a **negative exponential** curve.

The output comes within 36.8% (which is given in Problem Q3-2) of its final value at $t = \tau = RC$.

So $v_{\text{out}}(t) = e^{-t/(RC)}$. Note that $s \times \mathcal{L}\{v_{\text{out}}\} = s/(s + (1/RC)) = H(s)$.