

ECE 209: *Circuits and Electronics Laboratory*

Notes for Lab 4 (Frequency Response of First-Order Active Circuits)

1. Comments on returned lab report.

- Put units on tables and figures and show individual **data points** (i.e., not just interpolation).
- In meters lab, **positive error** on R_v is a **good thing**. Manufacturer gives worst-case specification.

2. First-order *active* filters.

- *Active* filters allow for gain, simplicity, robustness, and can have hard “knees” without inductors.
- Use standard inverting/non-inverting OA configuration, but use (equivalent) Laplace-domain impedances instead of simple resistances.
- To quickly determine characteristic of filter (i.e., low-pass, high-pass, or bandpass) consider what happens to OA configuration’s “gain” at some sample frequencies.
 - In today’s lab, both filter’s have transfer function given by $-Z_F(s)/Z_I(s)$.
 - In the low-pass filter, $Z_I(s) = R_1$ and $Z_F(s) = R_2 \parallel (sC)^{-1}$.
 - * $Z_F(0) \approx R_2$ for low frequencies — LF gain is $-R_2/R_1$ (i.e., R_2/R_1 with -180° shift).
 - * $Z_I(j\omega) \approx 0$ for high frequencies — HF gain is $-0/R_1 \approx 0$ (with $-180^\circ - 90^\circ$ shift).
 - * First-order filter’s time constant τ must depend on C , but because V_- is a virtual ground, the output does not “feel” the effect of R_1 . So time constant $\tau = R_2C$.
 - * It is a low-pass filter with **passband gain** $K = -R_2/R_1$ and **time constant** $\tau = R_2C$:

$$H_{\text{LPF}}(s) \triangleq \frac{K}{\tau s + 1} = \frac{-\frac{R_2}{R_1}}{sR_2C + 1}.$$

- In the high-pass filter, $Z_I(s) = R_1 + 1/(sC)$ and $Z_F(s) = R_2$.
 - * $Z_I(0) \approx \infty$ (i.e., “open” for VLF) — LF gain is $-R_2/\infty \approx 0$ (with $-180^\circ + 90^\circ$ shift).
 - * $Z_I(j\omega) \approx R_1$ for high frequencies — HF gain is $-R_2/R_1$ (i.e., R_2/R_1 with -180° shift).
 - * First-order filter’s time constant τ must depend on C , but because V_- is a virtual ground, the input does not “feel” the effect of R_2 . So time constant $\tau = R_1C$.
 - * It is a high-pass filter with **passband gain** $K = -R_2/R_1$ and **time constant** $\tau = R_1C$:

$$H_{\text{HPF}}(s) \triangleq \frac{Ks}{s + \frac{1}{\tau}} = \frac{K\tau s}{\tau s + 1} = \frac{-sR_2C}{sR_1C + 1}.$$

- As in passive filters, **corner frequency** is where **output power** is **half** of **passband power**.
 - If power gain is $1/2$, then signal gain is $1/\sqrt{2}$. Note that $20 \log_{10} \sqrt{2} = 10 \log_{10} 2 \approx 3 \text{ dB}$.

3. Introduce and complete the *Frequency Response of First-Order Active Circuits* lab.

- If 741-type operational amplifier is not available, use 747 (two 741-type OAs on one chip).
 - 747 (and 741) part pinout on supplementary document.
 - **Note the supply rails!** Op. amps need **power** from **both sides** to be able to work.
 - Be sure to use **dual $\pm 5 \text{ V}$ supplies** with a **common ground**. Use $\pm 6 \text{ V}$ if you see clipping.
 - If you see a **lot of noise** on **OA output**, then add $1 \mu\text{F}$ (code 105) across each supply rail.
 - * Connect one capacitor from **positive supply to ground**.
 - * Connect one capacitor from **negative supply to ground**.
 - * Place capacitors **close** to operational amplifier pins and try to use short capacitor leads.
 - * When used in this configuration, these capacitors are called **bypass capacitors** because they provide an alternate path for high-frequency (i.e., noisy) current. The operational amplifier sees steady rails because the ripples are directed elsewhere.

- The 741 is a **SLOW** OA. Its **bandwidth** and **slew rate** may corrupt high-pass filter data.
 - The *bandwidth* is typically 1.5 MHz, but it can be as low as 437 kHz. So signals approaching this frequency may see **attenuation** from poles within the OA that were previously negligible become significant. So **the high-pass filter may look like bandpass filter**.
 - The *slew rate* (i.e., maximum “speed” of OA output) is $\sim 0.5 \text{ V}/\mu\text{s}$ (i.e., 500 kV/s).
 - * “Speed” (i.e., derivative) of $A \sin(2\pi ft)$ output is $2\pi Af \cos(2\pi ft)$. Maximum is $2\pi Af$.
 - * For the OA to be able to move quickly enough, $2\pi Af < 500 \text{ kV/s}$; so $f < (500 \text{ kV/s})/(2\pi A)$.
 - * In this lab, **passband gain** is ~ 3 (i.e., 100/33) and the input signal has a 0.5 V amplitude (i.e., 1 V_{pp}), and so

$$f < \left(500 \frac{\text{kV}}{\text{s}} \right) \frac{1}{2\pi(0.5 \text{ V})} \approx 159 \text{ kHz.}$$

- * Any frequencies greater than 159 kHz may look more **triangular** than sinusoidal.
 - When a device output swings at its maximum rate, it is said to be **slewing**.
 - Your *Lissajous figures* (i.e., XY-mode) may look strange in this region.
 - Do your best and use these OA limitations as part of hypotheses in your report about differences from theory.
- In second table (i.e., for *high-pass filter*), change **Calculated phase shift** from

$$-90 - \arcsin(\Delta y_{\text{intersection}}/V_{o,\text{pp}}) \quad \text{to} \quad \boxed{-180^\circ + \arcsin(\Delta y_{\text{intersection}}/V_{o,\text{pp}})}$$

- Resistor color codes: Black, Brown, ROYGBV, Gray, White correspond to **digits** 0–9
 - **Orange-Orange-Orange** = 33000 = 33 k Ω ; **Brown-Black-Yellow** = 100000 = 100 k Ω
- Capacitor codes are like resistor codes (digit₁/digit₂/number-of-zeros) but *typically* use unit pF
 - *Sometimes* 200 pF = 201, but when $< 1 \text{ nF}$, *sometimes* capacitance is codeless.
 - * In today’s lab 200 pF is printed as 200 (i.e., code 200 \neq 20 pF).
 - * Letters like K or M following the small capacitance are *tolerance codes* (i.e., not *units*).
- **In your report**, for **both filters**, make **semilog** plots of

- Frequency** (Hz) versus **deciBel gain magnitude** (i.e., $20 \log_{10}(V_{o,\text{pp}}/V_{i,\text{pp}})$)
 - Make **data points** clear with plot **markers** (e.g., use `semilog(x,y,'.-')`).
 - Compare to expected magnitude curve, which is

$$|H_{\text{LPF}}(j2\pi f)| = \frac{R_2/R_1}{\sqrt{(2\pi R_2 C f)^2 + 1}}$$

or

$$|H_{\text{HPF}}(j2\pi f)| = \frac{2\pi R_2 C f}{\sqrt{(2\pi R_1 C f)^2 + 1}}$$

- Consider plotting expected curve on top of data curve for easy comparison.
 - * In MATLAB, plot two curves using `semilog(x1,y1,'.-',x2,y2,'-')`.
 - * Alternatively, try using MATLAB’s `hold` on command.
- Frequency** (Hz) versus **“calculated phase shift”** (i.e., from data table)
 - Again, make data points clear.
 - Compare to expected angle curve, which is

$$\angle H_{\text{LPF}}(j2\pi f) = -180^\circ - \arctan(2\pi R_2 C f)$$

or

$$\angle H_{\text{HPF}}(j2\pi f) = -90^\circ - \arctan(2\pi R_1 C f).$$

Be consistent about use of degrees and radians — don’t mix them! (recall: $180^\circ = \pi$)

- Again, consider overlaying expected and measured results.

For each filter, the pair of graphs represents a **Bode plot** of the system. **Try** to present possible explanations for deviations from theory (e.g., hypothesize about the impact of OA bandwidth).

Sample Code

```

##### Data from Measurements

% Store the frequency, measured input Vipp, output Vopp, and Lissajous vertical
% intersection data (note: the sample data here will NOT match theory below).
f = [1 2 10 20 30 40 50 60 70 80 90 100]*100;
vipp = [2.0 2.0 2.0 2.0 2.0 2.0 2.0 2.0 2.0 2.0 2.0 2.0];
vopp = [1.996 1.984 1.694 1.245 0.937 0.739 0.607 0.513 0.443 0.390 0.349 0.314];
deltaY = [0.125 0.247 0.901 0.975 0.828 0.687 0.578 0.496 0.432 0.383 0.343 0.310];

% Calculate gain vector (in dB) and phase (./ is element-by-element division).
gaindB = 20*log10( vopp./vipp );
phase = -180 - asin(deltaY./vopp)*180/pi; % For LPF
% phase = -180 + asin(deltaY./vopp)*180/pi; % For HPF

##### Theoretical Predictions (from transfer function)

% For theoretical curves, 1000 j-omega points in frequency range.
ftheory = linspace( min(f), max(f), 1000 );
s = j*2*pi*ftheory;

% For transfer function, store R and C values (change as necessary!).
R1 = 33000; R2 = 100000; C = 200e-12;

% Evaluate LPF transfer function at each ftheory.
H = -(R2/R1)./(s*R2*C + 1); % For LPF
% H = -R2*C*s./(s*R1*C + 1); % For HPF

% Find theoretical gain (dB) and phase (degrees).
gaintheorydB = 20*log10( abs(H) );
phasetheory = angle(H)*180/pi - 360; % For LPF (delay semantics)
% phasetheory = angle(H)*180/pi; % For HPF

##### Bode plot of measurements and expectations

##### Magnitude subplot: Measured and theoretical overlaid

% Put magnitude plot in top row of 2 row by 1 column figure.
subplot(2,1,1);
semilogx( f, gaindB, '-.', ftheory, gaintheorydB, '--' ); % dB Gain
grid on; % Add a grid

% Add axis labels (with units!) and title.
xlabel('Frequency (Hz)'); ylabel('Gain (dB)'); title('Gain magnitude');

##### Phase subplot: Measured and theoretical overlaid

% Put phase plot in bottom row of 2 row by 1 column figure.
subplot(2,1,2);
semilogx( f, phase, '-.', ftheory, phasetheory, '--' );
grid on;

% Add axis labels (with units!) and title.
xlabel('Frequency (Hz)'); ylabel('Phase shift (degrees)'); title('Phase shift');

% Use the figure's "File" menu to save the figure in a desirable
% file format (e.g., EPS or PNG) for inclusion in your report.

```