

# ECE 209: *Circuits and Electronics Laboratory*


## Notes for Lab 6 (Nonlinear Circuits: Diode and Transistor Switch)

1. This lab strays a little from signals and systems into circuits.


- Controls, signals, and communications engineers use abstract blocks. **Gross** oversimplification:
  - Signals and systems: analyze mathematical descriptions to determine impact on waveforms (input **and** output) (ECE 351/352/600).
  - Communications: How to change **input** to communicate over given channel (ECE 501/508).
  - Controls: How to adjust system for desired **output** (ECE 551/557).
- Circuits people implement blocks with *physical devices* (ECE 323/327/628).
- Materials people use *physical properties* to make devices (ECE 331/432/637).
- Physicists do experiments (i.e., **science**) to describe behavior of physical world.

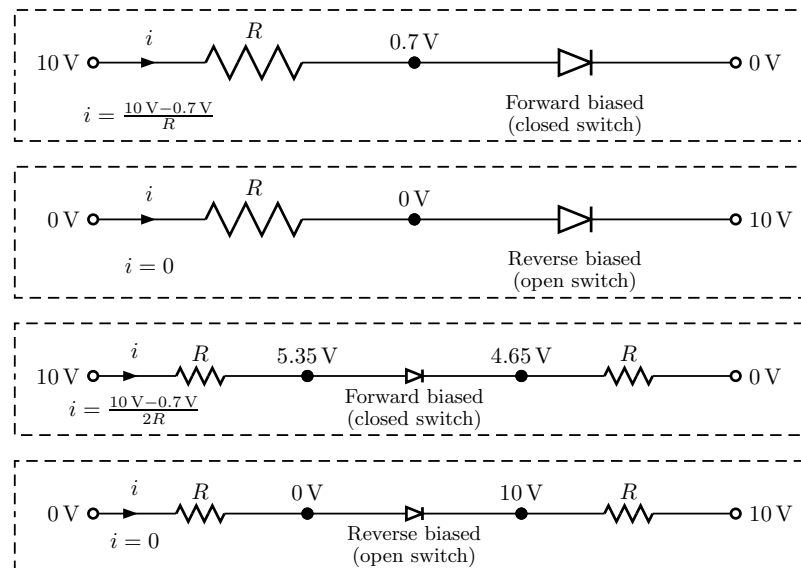2. Nonlinear circuits ( $v$  not linearly related to  $i$ ,  $i'$ , or  $\int i$ )


- A **diode** is a ***pn*-junction**; it joins a “*p*-type material” with an “*n*-type material.”
  - The *p*-type material is **neutral**, but its covalent lattice is incomplete; it *lacks* electrons in spots. Those spots where it is lacking are called “holes” and they act like positive charges.
  - The *n*-type material is **neutral**, but there are **more** electrons than needed for covalent lattice.
  - When the two materials are joined, *p*-type “holes” diffuse into the *n*-type material and *n*-type electrons diffuse into the *p*-type material (like different colored gasses mixing).
  - Diffusion causes the *n*-type material to become positively charged and the *p*-type material to become negatively charged. This **dipole** creates a force that **stops** further diffusion.
  - By applying a voltage to cancel the dipole, diffusion can continue and current will easily flow through the diode like a closed switch.
  - For **silicon diodes at room temperature**,  $\sim 0.7$  V of “forward bias” turns off dipole.
    - \* Picture spring-loaded ball check valve — small forward “cracking pressure” opens valve.
    - \* We use [1N914/1N4148](#) diodes —  $v_D \approx 0.7$  V @  $i_D \geq 10$  mA;  $v_D \approx 0.6$  V @  $i_D \approx 1$  mA.
      - In today’s lab,  $i_D$  will be slightly **less than** 1 mA, and so  $v_D < 0.6$  V (e.g., 0.5 V).
  - Diode symbol indicates direction of forward bias (arrow pointing in direction of current flow) — current flows from *p* to *n*.



- A **bipolar transistor** is a sandwich of three alternating types of semiconductor (*npn* or *pn*).
  - Current through device is amplified version of (forward-biased) *pn*-diode current.
    - \* Middle region is called **base**.
    - \* Complementary section of *pn* diode is called **emitter** (symbol arrow indicates emitter).
    - \* Other region is called **collector**.
  - For transistors in our lab, base current is amplified by  $\sim 100$ :
    - \* For *npn*, base current  $i_B$  flows from *p* to *n*; collector current  $i_C \approx 100i_B$  from *n* to *n*.

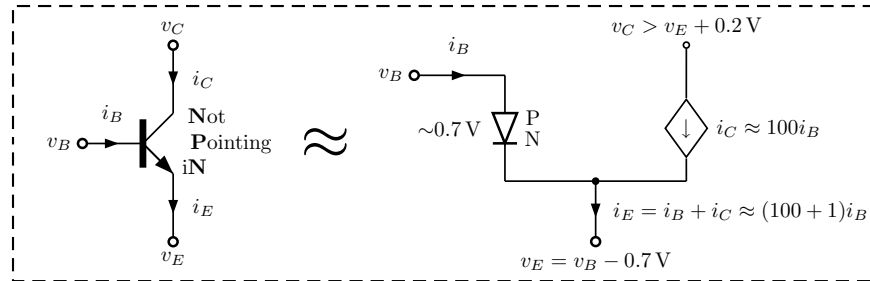

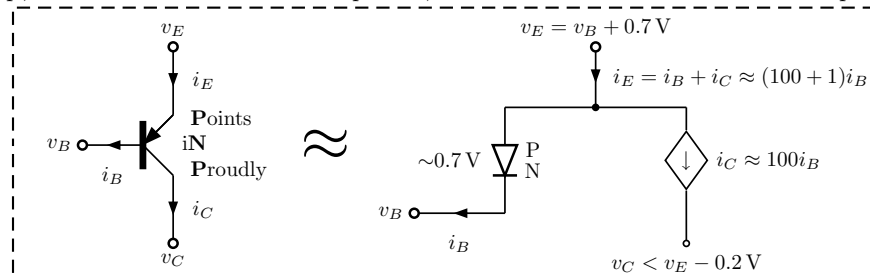- \* For *pn*, base current  $i_B$  flows from *p* to *n*; collector current  $i_C \approx 100i_B$  from *p* to *p*.



- \* Collector-to-emitter region acts like **resistor** that *tries* to adjust to ensure  $i_C \approx 100i_B$ .
  - A **transistor** is a **transfer** (variable) **reistor**.
  - Also called a *transconductance* (variable) resistor, but the justification for that use is outside the scope of this class.
  - Transistor can only act like *positive resistance*. That is, when  $i_B$  gets too large, transistor acts like a *short circuit* between collector and emitter.
    - When  $i_B \gg 0$ , “saturation mode” puts “closed switch” between collector and emitter.
    - When  $i_B = 0$ , “cutoff mode” sets  $i_C = 0$  (note that  $i_B \geq 0$  always).
    - When  $i_B$  is small, “active mode” means  $i_C \approx 100i_B$  (not used today).
  - Just like diode, collector-to-emitter “switch” has a small voltage ( $\sim 0.2$ ) across it.
- Bipolar symbol has arrow showing position of diode.
  - \* *npn* symbol is **not pointing in**; *pn* symbol **points in proudly**.
- In this lab, we make  $i_B$  zero or so large that transistor is in its “switching” regions.
  - \* Collector-to-emitter is either “open” (cutoff:  $i_B = 0$ ) or “closed” (saturation:  $i_B \gg 0$ ).
  - \* “Active” mode *is* used in many *analog* applications (e.g., the 741 op. amp. — see [schem.](#)).

### 3. Introduce and complete the *Nonlinear Circuits: Diode and Transistor Switch* lab.

- Resistor color codes: Black, Brown, ROYGBV, Gray, White correspond to **digits** 0–9
  - Brown-Black-Red = 1000 = 1 k $\Omega$ ; Brown-Black-Orange = 10000 = 10 k $\Omega$
- Part pinouts handout has **top views**; book shows bottom views.
- **In your report**, try to explain different regions of curves in terms of switches turning on/off.
  - Remember that conducting **diode** (i.e., “closed switch”) has 0.5~0.7 V drop across it.
  - Remember that conducting **transistor** (i.e., “closed switch”) has  $\sim 0.2$  V drop across it.
- For **part 3**, give **theoretical** and **actual**  $V_{s1,s2}$  values for *both* designs (i.e., Figures 4 and 5).