

ECE 209: Circuits and Electronics Laboratory

Operational Amplifier Basics: It's Not Black Magic; It's Negative Feedback*

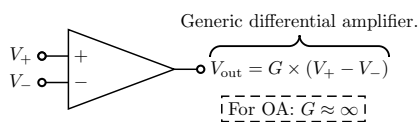


Figure 1: Operational amplifier (OA) alone.

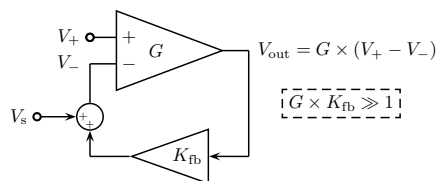


Figure 2: OA with negative feedback.

At the most basic level, an *operational amplifier* (OA) is a special kind of *differential amplifier* like the one shown in [Figure 1](#); the output is a scaled version of the difference between its two inputs. The special feature of an operational amplifier is that its *gain* is extremely large. In fact, it is so large that an operational amplifier is *useless* as a typical differential amplifier. As Horowitz and Hill¹ say, you should “think of an op-amp as *fodder* for feedback.”

An operational amplifier will almost always be used in a *negative-feedback* configuration like the one shown in [Figure 2](#). A *voltage divider* is commonly used to implement the feedback, but any connection that provides this kind of connection between the OA output and the V_- input will suffice². In this configuration,

$$\begin{aligned} V_- &= V_{\text{out}}K_{\text{fb}} + V_s \\ &= (V_+ - V_-)GK_{\text{fb}} + V_s \\ &= V_+GK_{\text{fb}} - V_-GK_{\text{fb}} + V_s, \end{aligned}$$

and so

$$V_- (1 + GK_{\text{fb}}) = V_+GK_{\text{fb}} + V_s$$

and

$$V_- = \frac{V_+GK_{\text{fb}}}{1 + GK_{\text{fb}}} + \frac{V_s}{1 + GK_{\text{fb}}}.$$

However, because GK_{fb} is very large, V_s has negligible impact on V_- , and V_- tends to follow V_+ . That is,

$$\boxed{V_- \approx V_+} \quad \text{because } GK_{\text{fb}} \text{ is very large.} \quad (1)$$

In other words, the operational amplifier *monitors* the difference between V_- and V_+ . If V_- strays from V_+ by even a small amount, the operational amplifier compensates appropriately to close the gap between them.

Because the operational amplifier ensures that V_- is identical to V_+ , it also ensures that

$$\boxed{V_{\text{out}} \approx \frac{V_+ - V_s}{K_{\text{fb}}}.} \quad (2)$$

So with clever choice of V_s (e.g., 0 V or a known signal) and feedback gain K_{fb} (e.g., some sub-unity gain from a voltage divider), the operational amplifier will ensure some useful relationship among V_{out} , V_+ , and V_s regardless of what else is connected to V_{out} . So an operational amplifier provides a *low-impedance output* that has the ability to *track* some other high-impedance output; we can avoid *loading* parts of our circuits by *buffering* them with an OA. Also, as in [Figure 3](#), we can *amplify* or *filter* signals using [Equation \(2\)](#).

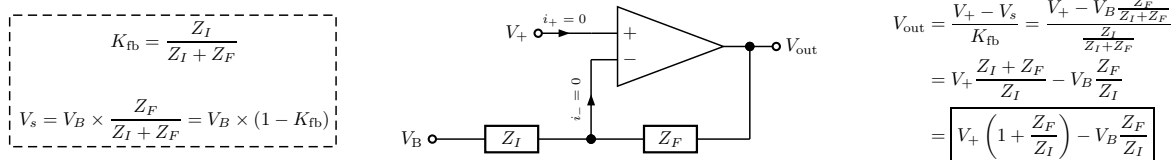


Figure 3: Typical ideal OA circuit. Uses voltage divider for feedback.

*Document from <http://www.tedpavlic.com/teaching/osu/ece209/>. Source code at <http://hg.tedpavlic.com/ece209/>.

¹The *Art of Electronics* (2nd edition) by Paul Horowitz and Winfield Hill. Cambridge University Press, 1989. Page 176.

²In fact, even many nonlinear gains (e.g., K_{fb} gains that vary with the output level) will suffice.