

# Choosing an Output for Maximum Power: Impedance Matching

## Abstract

Audio amplifiers warn users that speaker loads should be matched to the output impedance of the speaker drivers. Here, we explore why that is the case.

Consider the Thévenin equivalent in [Figure ZM-1](#).

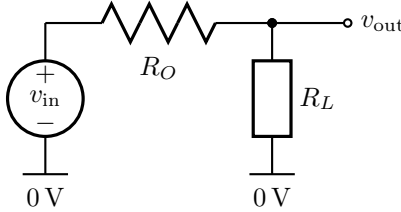


Figure ZM-1: Thévenin equivalent for voltage source (e.g., audio amplifier output).

The output voltage seen at the load is just a divided version of the input, and the power delivered to the load  $P_{out}$  is  $v_{out}^2/R_L$ . So

$$P_{out} = \frac{v_{out}^2}{R_L} = \frac{\left(\frac{R_L}{R_O + R_L} v_{in}\right)^2}{R_L} = \frac{R_L}{(R_O + R_L)^2} v_{in}^2. \quad (1)$$

For a fixed output resistance, a low load resistance will cause the divider to deliver very little potential to the load (and dissipate much power in the amplifier, possibly damaging it). Similarly, a high load resistance will deliver very little current to the load. Because power is the product of current and potential, there should be some intermediate load resistance that maximizes power delivered to the load.

## Finding the Optimal Output Resistance

For a fixed load resistance  $R_L$ , let's find the optimal output resistance  $R_O^*$ . It's clear that [Equation \(1\)](#) is a monotonically decreasing function of  $R_O$ . That is, for a fixed  $R_L$ ,  $P_{out}$  decreases as  $R_O$  increases. So the optimal output resistance is  $0\Omega$  and the corresponding power delivered is  $v_{in}^2/R_L$ . This result is both unsurprising and unrealistic.

## Finding the Optimal Load Resistance

Now, let's fix output resistance  $R_O$  and calculate the optimal load resistance  $R_L^*$ . We know that  $R_L^* > 0$ , and so the partial derivative of  $P_{out}$  with respect to  $R_L$  should be zero at  $R_L = R_L^*$ . In particular,

$$\left. \frac{\partial P_{out}}{\partial R_L} \right|_{R_L=R_L^*} = \left( \frac{-2R_L^*}{(R_O + R_L^*)^3} + \frac{1}{(R_L^* + R_O)^2} \right) v_{in}^2 = 0,$$

and so, assuming that  $v_{in} > 0$ ,

$$\frac{-2R_L^*}{(R_O + R_L^*)^3} = \frac{1}{(R_L^* + R_O)^2}.$$

Thus,

$$2R_L^* = R_L^* + R_O.$$

So  $R_L^* = R_O$ . To verify, note that because  $R_O > 0$ ,

$$\left. \frac{\partial^2 P_{out}}{\partial R_L^2} \right|_{R_L=R_L^*=R_O} = \frac{-2(R_L^* - 2R_O)}{(R_O + R_L)^4} = -\frac{1}{8R_O^3} < 0,$$

and so  $R_L^* = R_O$  is a maximum point (in fact, it's a global maximum). Note that the local "steepness" (i.e., convexity) of  $P_{out}$  around  $R_L = R_L^* = R_O$  increases greatly as output impedance decreases, so impedance matching is less important for high impedance outputs (i.e., the high output impedance will dominate the low power delivery, like a current limiter<sup>1</sup>).

<sup>1</sup>Note that current limiters are typically implemented as current sources that are turned on above a certain limit. Not surprisingly, a current source has infinite input impedance.