

ECE 327: *Electronic Devices and Circuits Laboratory I*

Procedure for Lab 5 (Analog-to-Digital Conversion (ADC) Lab)

SEE LAB BOOK. The questions you must answer in your report are given in the book.

Bypass capacitors: Unless otherwise noted, **bypass capacitors** terminate at $0 V_{DC}$.

Construction: **YOU WILL KEEP EVERYTHING** that you build in this laboratory. Build your circuits to be **clean, accessible, and COMPACT. TRY TO BUILD ENTIRE TRANSMITTER IN SAME BREADBOARD “COLUMN.”** Be sure to make the **LSA input**, **LSA output**, and **PWM output** **EASY TO FIND** in later laboratories; these signals are used often.


0. **BY NOW**, you should be using a $10 V_{DC}$ regulated supply for the *transmitter*. If you have not constructed your regulator. See the supplementary text for details. To ensure good performance, pay attention to bypass capacitors. **Everything** you build today will use this **regulated rail**.

1. Design, build, and test the level-shifter amplifier (LSA)

- See supplementary text for LSA schematics – **Use 10 V and 0 V supply rails**
 - Choose an LSA (the OA LSA is **recommended**) — for tuning, **USE potentiometers!**
 - * For the OA LSA, the C_B bypass capacitor and the **LM741** OA are **recommended**
 - * For the transistor-based LSA, use the “Good LSA” (i.e., attenuate signal first)
 - A **small bypass capacitor** (e.g., $0.1 \mu F$ ceramic) at $10 V_{DC}$ pin improves *PSRR*
 - **TO PREVENT EXPLOSIONS**, avoid **polarized** (e.g., electrolytic) **capacitors**
 - * Using **high input resistances** allows you the use of smaller coupling capacitors
 - * **Alternative:** combine small ceramic capacitors (e.g., use two $1 \mu F$ in parallel for $2 \mu F$)
 - * Make sure cathode (i.e., “negative” end) connected to lower DC voltage
 - * **Stand back from circuit** for a few seconds after turning on power
 - * **Be prepared** to turn supply off if a capacitor explodes
 - **LSA input** and **LSA output** are frequently used; **MARK THEM FOR EASY ACCESS**
- Generate a **sine wave** as a test input
 - Input (oscilloscope channel 1 at $2 V/div$ with ground on second-highest grid line):
 - * Frequency: $5 kHz$ (**after tuning**, try signals from $20 Hz$ to $15 kHz$)
 - * Amplitude: $1 V$ (i.e., $2 V_{peak-to-peak}$) — enable **Ampl -20dB** on *old* function generators
 - * DC offset: $0 V_{DC}$ (**after tuning**, try **small** offset; **careful** with electrolytic capacitors)
 - **Expected output** (scope channel 2; $2 V/div$; ground on lowest grid line): $-3 \times input_{AC} + 5 V$
 - * Frequency: Same as input (e.g., $5 kHz$)
 - * Amplitude: $3 V$ (i.e., $6 V_{peak-to-peak}$, but *inverted* with respect to input)
 - * DC offset: $5 V_{DC}$ (i.e., signal swings from $2-8 V$)
 - * **No phase shift:** If you see phase shift, your input capacitor and/or resistor are *too small*
 - Setup oscilloscope measurements
 - * Use **Quick Meas** on **Source** **1** (i.e., **input**) to show **Peak to Peak** (should be $2 V$)
 - * Use **Quick Meas** on **Source** **2** (i.e., **output**) to show **Peak to Peak** (should be $6 V$)
 - * Use **Quick Meas** on **Source** **2** (i.e., **output**) to show **Average** (should be $5 V_{DC}$)
 - * For cleaner measurements, turn on **Averaging** under **Acquire** (use **low** **#** of samples)
 - * To reduce output noise, use power supply *bypass capacitors* at regulator, clock, and LSA
 - **Tune gain and offset** until output is correct (again, **use potentiometers!**)
 - **SAVE A PLOT** showing **input**, **output**, and **measurements** on same screen
 - Some **possible** discussion topics for report:
 - * How does DC offset of input affect output?
 - * How does frequency of input affect output?
 - * How does temperature affect performance? Better or worse with op. amp implementation?

 2. Design, build, and test pulse-width-modulation (PWM) circuit

- See book's Figure 5.7: Pulse-Width Modulator
 - For **every component**, use 0 V and **regulated** 10 V supply rails
 - * **NOTE:** $GND = V_{EE} = V_{SS} = 0\text{ V}$ and $V_{CC} = V_{DD} = 10\text{ V}$
 - See supplementary text for **ramp generator** schematics. Use your *true* clock period for “ T .”
 - * Choose one of the two circuit options
 - * **USE POTENTIOMETER** for R_1 – R_2 divider or R_E resistor
 - * Use **CD4066** for switch — **TEST SWITCH BEFORE** connecting to circuit
 - **First**, ensure that $V_{SS} = 0\text{ V}$ and $V_{DD} = 10\text{ V}$
 - Construct the testing circuit shown below, where $R = 1\text{ k}\Omega$



- For safety, use a 1–1.5 k Ω resistor for CONTROL connections (i.e., instead of simple “wire”)
- For 0 V control, use DMM to verify switch *input* sees 10 V and switch *output* sees 0 V
- For 10 V control, use DMM to verify *input and output BOTH* see **the same** 5 V
- **TEMPORARILY** connect control to 30 kHz clock and verify **no switch delay**
- Repeat until **ONE** working switch is found — only get a new chip if **ALL** switches fail
- **DISCONNECT switch testing circuit** (but leave V_{SS} and V_{DD} connected)
- * Calculate desired $i_C = C dv_C/dt$ for appropriate ramp slope (ramp slope is dv_C/dt)
 - Pick slope so that $(8\text{ V})/(T - 6\ \mu\text{s}) \leq dv_C/dt \leq .333\text{ V}/\mu\text{s}$ for your *true* clock period T
 - Start with $C = 2.2\text{ nF}$ (code: 2n2 or 222) — in most cases, this value is a good choice
- * Pick biasing circuit and R_E to implement i_C source
 - Make biasing circuit, R_E , or both **TUNABLE**
- * To **TEST** your ramp generator, **temporarily** connect its *Reset* input (i.e., the FET control) to a 30 kHz 0–10 V clock (e.g., **from your 555 circuit** or a function generator)
 - The ramp generator output should be a train of **ramps and resets**
 - If ramps are **noticeably round** and resets **vertical**, try *reconfiguring* for a *higher* C
 - If ramps are **linear** and resets **very curved**, try *reconfiguring* for a *lower* C
 - **DO NOT TUNE your ramp slope at this time**
 - **DISCONNECT Reset** from clock when done testing
 - *Reset* will eventually be tied to \overline{Q} on your *JK* flip-flop
- * **OPTIONAL:** Use **small (ceramic) bypass capacitor** at supply pin (i.e., 10 V_{DC} input)
- Use **LM311** voltage comparator with *open-collector* output
 - * **CAUTION:** Pin-out *similar* to op. amp., but *inputs are swapped*
 - * **CAUTION:** There is a **GROUND** pin **AND** a **V-**. Connect them **BOTH** to 0 V.
 - * Output **must be pulled-up** to 10 V_{DC} with a 1 k Ω resistor (code: brown-black-red)
 - **OPTIONAL:** Use **small (ceramic) bypass capacitor** at resistor's 10 V_{DC} supply pin
 - * Non-inverting input (i.e., “+” input) tied to **ramp generator output's** capacitor voltage
 - * Inverting input (i.e., “–” input) is **PWM input**, so **MARK IT FOR EASY ACCESS**
 - * **DO NOT** connect the **LSA output** to the **PWM input**
 - You're not ready for that **YET**

- Use a *JK* flip-flop from **CD4027** (or *D*-type **CD4013**; pin-out: swap *J* & *K* pins for *D* pin)
 - * Connect power rails so that $V_{DD} = 10\text{ V}$ and $V_{SS} = 0\text{ V}$
 - * Configure so output *Q* goes **high on clock edge**:
 - *CLK* tied to 30 kHz clock from previous lab (i.e., pin 3 of **555**)
 - *J* (or *D*) tied to 10 V (i.e., *high*)
 - *K* tied to 0 V (i.e., *low*)
 - * Configure so output goes **low asynchronously** by comparator output:
 - *S* tied to 0 V (i.e., *low*)
 - *R* tied to comparator output
 - * Configure so ramp generator is reset when output is *low*:
 - \overline{Q} tied to ramp's “reset” input (i.e., the **CD4066** switch control)
 - * For safety, use a 1.5 k Ω resistor (code: brown-green-red) to make this connection
 - * **OPTIONAL**: Use **small (ceramic) bypass capacitor** at V_{DD} pin (i.e., 10 V_{DC} input)
 - * Output *Q* is **PWM output**, so **MARK IT FOR EASY ACCESS**
- Test and tune PWM circuit
 - **Apply** 2 V_{DC} to 8 V_{DC} to **PWM input** (i.e., comparator's “–” input)
 - * Generate with second DC supply output **OR** the *wiper* of a potentiometer between rails
 - Connect oscilloscope to circuit
 - * Channel 1: Capacitor waveform (i.e., **ramp output**) at 2 V/div
 - * Channel 2: **PWM output** at 10 V/div
 - * Set oscilloscope **trigger** **Edge** for **RISING** transitions on source **2**
 - * **Separate** channels: put ramp ground on lowest grid line and PWM ground on 2nd highest
 - Use **Quick Meas** to measure: **Maximum** of **1**, and **+ Width** and **– Width** of **2**
 - Manually vary **DC input** slowly (i.e., oscillate from 2 V to 8 V) and observe:
 - (i) Slope of ramp
 - (ii) Maximum height of ramp (compared to input)
 - (iii) Relationship (in time) between ramp and PWM output
 - (iv) **+ Width** (i.e., time per period that output is **high**)
 - (v) **– Width** (i.e., time per period that output is **low**)
 - **TUNE** **ramp generator current** (i.e., ramp slope) until **ALL** of the following:
 - (i) **IMPORTANT**: The sum of **+ Width** and **– Width** is **equal** to your **clock period**
 - * If it is too *large*, then *greatly increase slope* until compliant
 - (ii) **+ Width** for constant 2 V_{DC} PWM input is 6 μs or greater
 - (iii) **– Width** for constant 8 V_{DC} PWM input is 6 μs or greater
 - **AFTER TUNING**, show **ramp output** and **PWM output** at both extremes
 - * Use **Quick Meas** to show **+ Width**, output **– Width**, and ramp **Maximum**
 - * For 2 V_{DC} input, **SAVE A PLOT** showing **PWM**, **ramp**, and **measurements**
 - * For 8 V_{DC} input, **SAVE A PLOT** showing **PWM**, **ramp**, and **measurements**
 - Using **Cursors**, **DETERMINE THE SLOPE** (in V/ μs units) of the ramp output
 - * **MAKE SURE** that cursor **Source** is set to your **ramp channel** (i.e., **1**)!!!!
 - * **SAVE A PLOT** showing **ramp** and **Cursors** with slope information (i.e., ΔX , ΔY)
- Some **possible** discussion topics for report:
 - What is the relationship between input and ramp output? ... ramp output and PWM output?
 - What determines the slope of the falling edge of the ramp? Why is it not totally vertical?
 - Why are 2 V_{DC} and 8 V_{DC} important inputs?
 - How does temperature affect performance? (hint: consider ramp generator's current source)
 - * An **LM317** can be used as a current source — assuming $DO \approx 1\text{ V}$, why can't we use it?

3. Connect LSA to PWM

- *Disconnect* 2–8 V_{DC} input from **PWM input** (i.e., comparator’s “–” input)
- Connect **LSA output** (i.e., op. amp. output) to **PWM input** (i.e., comparator’s “–” input)
- Generate a **sine wave** as a test input to **LSA**
 - LSA Input:
 - * Frequency: 5 kHz
 - * Amplitude: 1 V (i.e., 2 V_{peak-to-peak}) — enable **Ampl -20dB** on *old* function generators
 - * DC offset: 0 V_{DC}
- View *LSA output* and *ramp generator output*
 - Channel 1: **LSA OUTPUT** at 2 V/div
 - Channel 2: **ramp generator output** at 2 V/div
 - **ALIGN both channel grounds** on lowest grid line
 - Set oscilloscope **trigger** **Edge** for source **1**
 - * Adjust **trigger level knob** or **trigger filtering** (see **Mode**) until **channel 1** stabilizes
 - * The input and output are naturally **asynchronous**, so channel **2** MAY MOVE
 - Note the relationship between the two channels. TRY VARIOUS **horizontal (time) scales**
 - Press **Run/Stop** or **Single** to pause display
 - **SAVE A PLOT** and **THEN** toggle **Run/Stop** back to **green**
- View *ramp generator output* and *PWM output*
 - Channel 1: **ramp generator output** at 2 V/div
 - Channel 2: **PWM output** at 10 V/div
 - Set oscilloscope **trigger** **Edge** for **RISING** transitions on source **2**
 - **Separate** channels: put ramp ground on lowest grid line and PWM ground on 2nd highest
 - Press **Single**. Note the relationship between the two channels
 - **SAVE A PLOT** and **THEN** toggle **Run/Stop** back to **green**
- View *LSA INPUT (NOT output!)* and *PWM output*
 - Channel 1: **LSA INPUT (NOT output!)** at 2 V/div
 - Channel 2: **PWM output** at 5 V/div
 - Set oscilloscope **trigger** **Edge** for source **1**
 - * Stabilize **channel 1** (**2** can move) with **level knob** or **filtering** (see **Mode**)
 - **Separate** channels on the screen
 - Press **Single**. Note the relationship between the two channels
 - **SAVE A PLOT**
- Some **possible** discussion topics for report:
 - What are the relationships among the LSA input, ramp output, and PWM output?
 - * Given an input signal, how can the other signals be predicted?
 - * What is the relationship between input amplitude and output pulse width?
 - Given that a walkman output has a 15 kHz bandwidth, what is the rationale for using a 30 kHz carrier in the PWM circuit?
 - How does temperature affect performance? (hint: how does the ramp generator work?)
 - Why (and how) does the *C* value change the *curviness* of the “sawtooth” characteristics?
 - The output of this circuit can be viewed as a string of 0’s and 1’s (i.e., it takes 2 states). However, it is not an ADC. Why not? (hint: can you *count* the number of “adjacent” 1’s?)
 - The PWM circuit could be called an ADC if the positive width of each pulse was counted (e.g., in terms of high-speed clock cycles). What would set the *resolution* of such an ADC?